
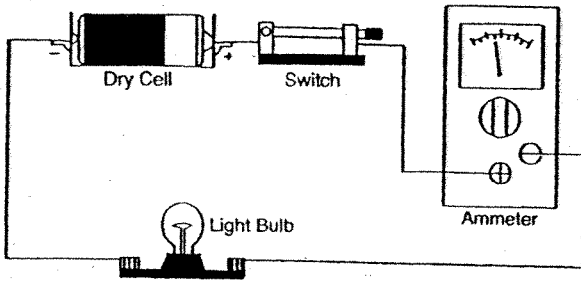


Draw the following circuits using electrical symbols.


1.

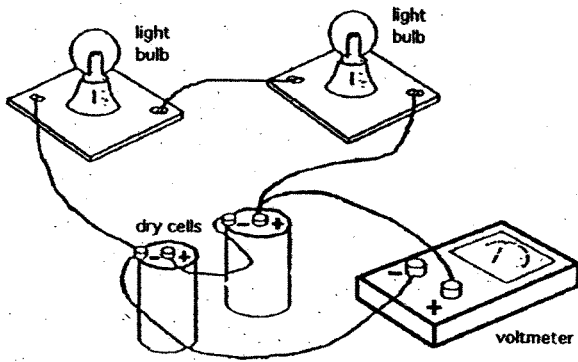

2.



3.

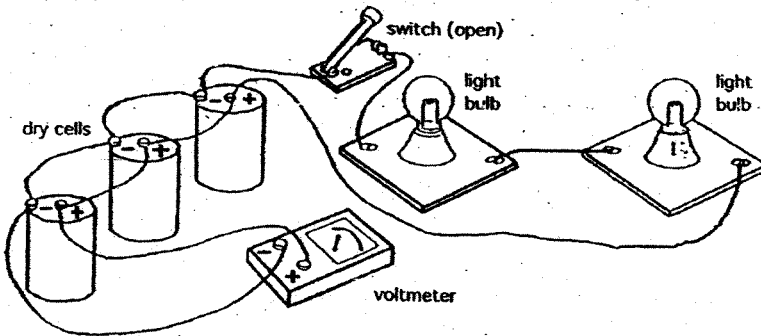

4.

